

2017 EOU E&M Quiz**Multiple Choice**

Identify the choice that best completes the statement or answers the question.


- _____ 1. In order for there to be a flow of charge from one place to another, there must be a
- conductor, such as a wire, connecting the two places.
 - potential difference between the two places.
 - Both A and B above
- _____ 2. Atomic nuclei of almost all elements consist of
- protons and neutrons.
 - neutrons and electrons.
 - protons and electrons.
 - only protons.
 - only neutrons.
- _____ 3. When two light bulbs are connected in series, the
- same amount of current always flows through each bulb.
 - current through each light bulb is proportional to the resistance of the bulb.
 - neither A nor B
- _____ 4. Electrical resistance is measured in
- amperes.
 - joules.
 - watts.
 - volts.
 - none of the above
- _____ 5. An ampere is a
- current.
 - unit of resistance.
 - unit of current.
 - voltage.
 - type of charge.
- _____ 6. When resistors are put in parallel with each other their overall resistance is
- the same as the resistance of one of the resistors.
 - smaller than the resistance of any of the resistors.
 - larger than the resistance of any other resistor.
- _____ 7. Two like charges
- attract each other.
 - must be neutrons.
 - neutralize each other.
 - have no effect on each other.
 - repel each other.
- _____ 8. Two charged particles held near each other are released. As they move, the acceleration of each decreases. Therefore, the particles have
- opposite signs.
 - the same sign.
 - charges that can not be determined.

2017 EOU E&M Quiz

Circuit Problem Solving

Solve the problem using the scratch paper provided and then identify the choice that best answers the question.

Use the following diagram and data for questions 9 – 12

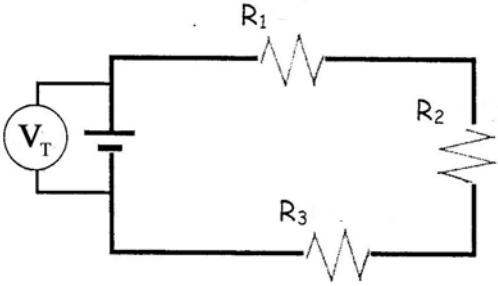	<table border="1" style="width: 100%; border-collapse: collapse;"> <tr> <td style="padding: 5px;">$V_T = 70\text{v}$</td> <td style="padding: 5px;">$R_1 = 10\ \Omega$</td> </tr> <tr> <td style="padding: 5px;">$R_2 = 35\ \Omega$</td> <td style="padding: 5px;">$R_3 = 5\ \Omega$</td> </tr> </table>	$V_T = 70\text{v}$	$R_1 = 10\ \Omega$	$R_2 = 35\ \Omega$	$R_3 = 5\ \Omega$
$V_T = 70\text{v}$	$R_1 = 10\ \Omega$				
$R_2 = 35\ \Omega$	$R_3 = 5\ \Omega$				


9. What Kind of Circuit is this?
 - a. Parallel
 - b. Combo Parallel-Series
 - c. Combo Series-Parallel
 - d. Series
 - e. None of these

10. What is the Total Current in this circuit?
 - a. 1.4 amps
 - b. 2 amps
 - c. .5 amps
 - d. 0.3 amps
 - e. 1.6 amps

11. What is the Voltage drop across Resister #1?
 - a. 30 V
 - b. 14 V
 - c. 15 V
 - d. 7.5 V
 - e. 35 V

12. What is the Voltage drop across Resister #2?
 - a. 49 V
 - b. 12.5 V
 - c. 7.5 V
 - d. 10 V
 - e. 30 V

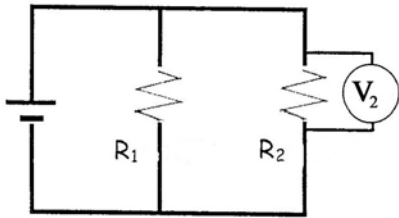13. What is the Voltage drop across Resister #2?
 - a. 10 V
 - b. 15 V
 - c. 10 V
 - d. 7 V
 - e. 30 V



$V_2 = 35\text{v}$	
$R_1 = 18\ \Omega$	$R_2 = 9\ \Omega$

14. What Kind of Circuit is this?

- a. Parallel
- b. Combo Parallel-Series
- c. Combo Series-Parallel
- d. Series
- e. None of these

15. What is the Total Current in this circuit?


- a. 7.5 amps
- b. 2 amps
- c. 5.8 amps
- d. 3 amps
- e. .3 amps

16. What is the Current through Resister #1?

- a. 7.5 amps
- b. 2 amps
- c. 2.5 amps
- d. 3 amps
- e. 1.9 amps

17. What is the Current through Resister #2?

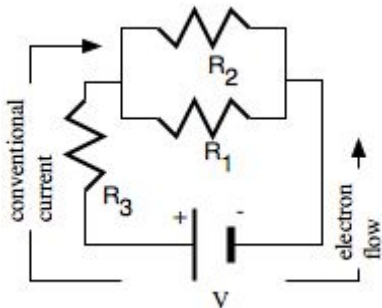- a. 3.9 amps
- b. 2 amps
- c. 2.5 amps
- d. 3 amps
- e. .3 amps



$V_T = 50\text{v}$	$R_1 = 10\ \Omega$
$R_2 = 20\ \Omega$	$R_3 = 25\ \Omega$

18. What is the Total Current in this circuit?

- a. 7.5 amps
- b. 2 amps
- c. 2.5 amps
- d. 1.6 amps
- e. .5 amps

19. What is the Current across Resister #2?

- a. 7.5 amps
- b. 2 amps
- c. 2.5 amps
- d. 1.6 amps
- e. .5 amps

20. What is the Voltage drop across Resister #3?

- a. 155 V
- b. 39.5 V
- c. 22.6 V
- d. 10 V
- e. 50 V